

Video 1: The Multimeter

1. Introduction to Electric Variables & Multimeter:

Understood the resistance, voltage, current & and their relationship which is denoted by Ohm's Law. Multimeter is an electrical component which is used to measure electric parameters.

2. Measuring Resistance with Multimeter:

There are two probes, one is black which is connected to common socket and other is red which is connected to voltage or current socket. There is a continuity feature in multimeter which indicates zero resistance and beeps if there are any cable breaks.

3. Measuring Voltage and Current:

Measured Voltage in parallel, red probe was connected to positive side and black one to the negative. Measured current in series, the red probe was connected to 10-amp socket because it always start with the high current socket because the other socket can only endure up to 500 Milliamps.

4. Multimeter issue:

If the multimeter isn't working, then replace its fuse to work properly.

Video 2: Dimming All Kind of LEDs

1. Controlling of LEDs Brightness:

LED brightness can be controlled by with or without the help of an Arduino microcontroller, which is called PWM (Pulse Width Modulation).

2. Techniques of Dimming:

lowering the voltage underneath the forward voltage level less current will be consumed and the LED gets darker, but usually fixed voltage sources are used. Another easiest solution would be

using potentiometer in series but there would generate some problems like wasting energy and being expensive.

3. Methods Of PWM:

Switches very fast between high and low voltage (e.g. 5V & 0V). There is a duty cycle, if it is 100% means LED is fully bright, when it is lowered the LED gets darker, e.g. 50% duty cycle means 2.5V perceived. Then we can get the signals in 2 ways, one is with the help of Arduino microcontroller: duty cycle 0% leads to a value of 0(0V) and duty cycle 100% leads to a value of 255(5V), the other one with a 555 Timer Chip: described as an 'easy to wire' ic, duty cycle is controlled by a potentiometer. Uses a MOSFET which acts as a switch that can handle larger currents and voltages than the signal-generating device itself.

4. Benefits of PWM:

Works with fixed voltage sources, avoids energy waste and cost associated with potentiometers for high power, Scalable for Higher Power Loads using a MOSFET.

Video 3: Programming an ATtiny + Homemade Arduino Shield:

1. Introduction of ATtiny 85 microcontroller:

The ATtiny 85 is a cost-effective alternative to the ATmega 328 for simple projects. The main summary is the utilization of the ATtiny85 as a more affordable and appropriately sized microcontroller for projects with limited I/O needs.

2. Programming Method: To program the ATtiny85, an Arduino Uno must first be transformed into an "Arduino ISP" programmer. This includes downloading the board data files for the ATtiny and uploading the "Arduino ISP" sketch to the Uno.

3. Pinout and I/O capabilities: The document outlines the I/O pins, memory, and available functionalities (analog input, PWM), while also addressing limitations, particularly the lack of built-in SPI hardware.

- 4. Programming Shield:** The custom shield's advantage is improvement over direct wiring. The shield constructs a programmer platform using male headers, an IC socket, and bridge wire, it is also added with female header pins so that it can eliminate wiring effort when programming.
- 5. Limitations:** There is a lack of hardware SPI support for WS2801 which can be overcome by using a 'bit-banged' emulated version of the protocol, another disadvantage of the ATtiny is that one cannot use all the functions of an Arduino.

Video 4: **Arduino + Bluetooth + Android = Awesome**

- 1. Components:** Used an Arduino Nano and a common Bluetooth module named HC-05.
- 2. Voltage incompatibility and Solution:** There was a voltage level difference between the Arduino (5V logic) and the Bluetooth module (3.3V logic). For the solution, a voltage divider circuit is required.
- 3. Wiring and Connection:** Detailed with the wiring process, specifically connected the connection of the Bluetooth module's transmit (TX) and receive (RX) pins to the Arduino and used the resistors for LED connections. There was also a connection of a module's RX pin to the middle of the voltage divider.
- 4. Use of Android App:** Used a "S2 terminal" android app for communication with the Bluetooth module.
- 5. Code and Customization:** Provided with a framework for the Arduino code, allowing users to easily customize "code word[s]" (like "red," "green," "blue") and the corresponding actions and response text.

- 6. Caution:** Always cut the TX and RX connections to the module when one uploads the code and it interferes with one another and it will not work.

Video 5: How to Multiplex

- 1. Concept:** Controlling many LEDs individually requires a significant number of I/O pins, often exceeding the capacity of typical microcontrollers like the Arduino Nano.
- 2. Matrix Wiring for Multiplexing:** The trick is to wire LEDs in a matrix format. This is done by connecting all the cathodes (negative pins) of LEDs in a column together and all the anodes (positive pins) of LEDs in a row together.
- 3. Limitation with Matrix Wiring:** While matrix wiring reduces connections, simply applying voltage directly to rows and ground to columns to light multiple LEDs simultaneously leads to unwanted LEDs illuminating due to the shared connections.
- 4. Solution:** lighting up each row (or column) individually, one after the other, in rapid succession.
- 5. Power Considerations:** Driving an entire row of LEDs simultaneously can draw significant current (up to 200 milliamps with 10 LEDs in a row).
- 6. P-Channel MOSFETs as Switches for Rows:** P-channel MOSFETs are used as switches to control the power supplied to each row. The microcontroller's I/O pins control the gate of the MOSFETs, effectively turning the rows on or off.
- 7. TLC5940 LED Driver IC for Columns:** TLC5940 is used to control the current flowing through the columns. This IC simplifies controlling multiple LEDs and can handle the necessary current.

- 8. Visual Demonstration of Multiplexing:** Increasing the "on time" of a row makes the multiplexing visible as individual rows lighting up sequentially rather than a single complete picture.

Video 6: Standalone Arduino Circuit

- 1. Embedding the ATmega328p:** breaking the ATmega328p Microcontroller free from its Arduino prison and embedding it into a circuit. This allows for projects where the physical size or form factor of a standard Arduino board is prohibitive.
- 2. Constructing Circuit:** Outlining the necessary external components and connections to get the ATmega328p running without a full Arduino board.
- 3. Generating External Clock:** provided an external clock signal, typically provided by a 16 MHz crystal and two 22 pF capacitors. An alternative is to use the internal 8 MHz oscillator, but this requires uploading a different bootloader.
- 4. Connection and Mapping:** Connected specific pins (7, 20, 21) to 5 volts, while others (8, 22) are connected to ground. A crucial point is that the digital and analog pin numbers used in Arduino sketches do not directly correspond to the physical pins on the ATmega328p.
- 5. Reprogramming:** Once it's in a standalone circuit, there are several ways to upload new code (sketches) to the ATmega328p.

Video 7: 7 Segment Display

- 1. Concept:** 7-segment displays are a little bit older technology, particularly suited for projects displaying limited numerical or alphabetical output.

- 2. Configuration:** The display consists of eight individual LEDs, seven for the bars and one for the decimal point. There are datasheets for pinout information and common anode and common cathode configurations.
- 3. Functioning Display Without a Microcontroller:** Controlling 7-segment displays using discrete logic ICs—specifically the BCD to seven-segment display driver (SN74LS247) and the 4-bit binary counter (SN74HC290), enables simple counting or number display without relying on an Arduino.
- 4. Functioning Display with an Arduino Microcontroller:** The use of 7-segment displays with an Arduino, especially for multi-digit setups, introduces multiplexing as a method to minimize the number of required Arduino pins.
- 5. Using a Dedicated IC for Multi-Digit Displays:** A specialized IC like the SAA1064 is recommended for controlling multi-digit displays with an Arduino, as it manages multiplexing and communicates via the I²C protocol, greatly reducing both the number of required Arduino pins and the processing power needed for display control.
- 6. Extra Components (Resistors, Capacitors, Transistors):** The schematics require specific components such as 220-ohm resistors for current limiting, a 2.2-nanofarad capacitor to set multiplexing speed, and BC337 NPN transistors for handling multiplexing.

Video 8: Everything about LEDs and current limiting resistors:

- 1. LED Parameters and the Need for Current Limiting:** LEDs have two crucial parameters: Forward Voltage (the voltage required across the LED for it to light up) and the Ideal Current (the amount of current needed for optimal brightness and

longevity). A typical LED might have a forward voltage of around 3.2 volts (though 3 volts is suggested as a more precise general value) and an ideal current of 20 milliamps. The resistor is necessary to limit the current flowing through the LED, ensuring it operates within its specified current range.

- 2. Calculating the Resistor Value using Kirchhoff's and Ohm's Laws:** Kirchhoff's Voltage Law is fundamental to determining the voltage drop across the resistor. In a simple series circuit with a power source, resistor, and LED, the sum of the voltage drops across the resistor and the LED must equal the power source voltage. Ohm's Law ($\text{Resistance} = \text{Voltage} / \text{Current}$) is used to calculate the required resistor value.
- 3. Resistor Power Rating:** Resistors have a power rating; this indicates the maximum amount of power the resistor can safely dissipate as heat. The power dissipated by the resistor is calculated using the formula: $\text{Power} = \text{Voltage} \times \text{Current}$.
- 4. Driving Multiple LEDs Efficiently:** Connecting LEDs in series is generally more efficient for driving multiple LEDs from a single power source, provided the total forward voltage of the series LEDs does not exceed the power source voltage. When connecting LEDs in series, the total forward voltage is the sum of the individual LED forward voltages. The current flowing through all LEDs in the series is the same.
- 5. Advanced Considerations:** The actual forward voltage and current draw of individual LEDs can vary, even within the same batch. The current consumption of an LED is exponential with respect to voltage. A small change in voltage can lead to a significant change in current, potentially damaging the LED. Even if the power source voltage is equal to the LED's forward voltage, using a small resistor is recommended to linearize the current

consumption. This makes the LED less susceptible to voltage fluctuations. Using a single resistor to drive multiple LEDs in parallel is problematic because the forward voltage of individual LEDs can vary. The most effective way to drive LEDs is in a constant current mode rather than a constant voltage mode. Dedicated constant current sources (e.g., using an LM317 or TLZ 5940) are superior for precise LED control, although they can have efficiency drawbacks.

Video 9: Diodes & Bridge Rectifiers

- 1. Diodes:** Diodes are widely used across electronic devices, from older linear power supplies to modern switching power supplies and a range of consumer electronics. The fundamental principle of a diode is that it allows current to flow in only one direction
- 2. Preventing Reverse Polarity:** Diodes can be used to protect circuits from damage caused by incorrectly connecting the power supply with reversed polarity. By placing a diode in series, if the polarity is reversed, no current will flow, safeguarding the circuit.
- 3. Voltage Drop Across a Diode:** Diodes exhibit a voltage drop when conducting current, which depends on the current draw and reduces the effective voltage delivered to the rest of the circuit, indicating they are not perfect switches.
- 4. RMS vs. Peak Voltage in AC:** AC voltage from a transformer is typically specified as RMS (Root Mean Square) voltage, which relates to the maximum or peak voltage by the formula: $\text{RMS voltage} = \text{Max Voltage} / \sqrt{2}$ for sine waves.
- 5. Smoothing DC with a Capacitor:** Adding a capacitor after a single-diode rectifier helps to smooth out the bumpy DC by storing charge during the peaks of the waveform and discharging during

the gaps. However, the output can still become bumpy when current is drawn.

- 6. Bridge Rectifier for Full-Wave Rectification:** A bridge rectifier, consisting of four diodes, provides a more effective way to convert AC to DC. By using a specific arrangement of diodes, the negative half of the AC waveform is "flipped" and added to the positive half, resulting in a more continuous, albeit still bumpy, DC output.

Video 10: **Digital to Analog Converter (DAC)**

- 1. The Need for DACs:** Digital devices operate on discrete digital logic levels (high/low, 0/1). To produce analog signals like sound waves, which are continuous in nature, a conversion process is required. DACs bridge this gap.
- 2. Resolution of DACs:** The "bit" value of a DAC determines its resolution, or the number of distinct voltage levels it can produce. A higher bit count allows for a greater range of possible output voltages and thus a more precise representation of the analog signal.
- 3. Building DAC & Generating Analog Waveforms:** A basic resistor ladder DAC is constructed using resistors to show how varying digital inputs produce corresponding analog output voltages. With a DAC, it is possible to generate various analog waveforms like ramp, triangle, and sine waves by systematically changing the digital input value.
- 4. Output Buffering:** Connecting a load, such as a speaker, directly to a simple DAC can cause the output voltage to collapse or change form. An operational amplifier (op-amp) configured as a voltage follower is essential to keep the output voltage stable when a load is connected.

- 5. Arduino's analogWrite () Function:** The analogWrite() function in Arduino generates a Pulse-Width Modulation (PWM) signal rather than a true analog output. Although it can be filtered to approximate an analog signal, it differs fundamentally from the output of a dedicated DAC.
- 6. External DAC Modules:** Pre-built external DAC modules, often communicating via protocols like I2C, provide a convenient way to add high-quality analog output capabilities to microcontrollers like Arduino.

Video 11: Sending SMS with Arduino || TC 35 GSM Module

- 1. Module Origin and Quality & Affordability:** The TC35 module originates from a reputable manufacturer, likely Siemens, known for reliable and functional products, while the surrounding board appears to be of Chinese origin, suggested by features like "beautiful solar joints" and the presence of a CDC Jack. The TC35 GSM module board is described as relatively inexpensive, with one unit acquired for \$23 and an even lower-priced option available at \$18.
- 2. Sim Card Preparation:** A prepaid SIM card should first be inserted into a smartphone to remove the SIM lock before placing it into the module's holder.
- 3. Powering the Board:** The board can be powered via the DC jack or VCC and ground pins. The presenter strongly recommends 5V due to the MAX232 IC, which is directly connected to VCC/ground and has a maximum endurance of 6V. Using 12V is possible but requires removing the MAX232. Using 5V also saves power.

- 4. Network Login Process:** The module requires a button press to initiate the network login. This can be automated by connecting the "right side" of the switch (which connects to ground to start the login) to an Arduino pin (specifically pin 10 in the example). Pulling this pin low initiates the login.
- 5. Communication Protocol (AT Commands):** The module communicates using "simple AT commands." These commands are listed in "at command reference." A basic test typing "a" and receiving "okay" confirms communication is working. Other basic information like network operator and signal strength can also be retrieved.
- 6. Arduino Wiring and Compatibility:** The wiring between the Arduino and the TC35 board is "super easy." Although the TC35 uses 3.3V logic levels, it is "compatible with the 5v signals of the ftdi and Arduino." The TX and RX pins on the board are described as having "messed up the labeling," requiring a reverse connection (TX to rxd0 and RX to txd0).
- 7. Sending SMS Program Logic:** The provided Arduino sketch demonstrates the process of sending an SMS. This involves opening the serial monitor, pulling the startup switch low, entering the SMS text, and finishing it with a "DOT at the end." The program then handles the transmission.
- 8. Future Applications:** The board is intended for use in building an alarm system that sends SMS notifications.

Video 12: Coils / Inductors (Part 1)

- 1. Importance of Coils:** Coils are highlighted as fundamental components, commonly found across a wide range of electronic devices and systems, alongside resistors and capacitors.

- 2. Magnetic Field Creation:** A fundamental principle is that current flowing through a wire generates a magnetic field around it, with the field's strength directly proportional to the current.
- 3. Induction:** Induction occurs when a voltage is generated in a conductor either by its movement through a magnetic field or by changes in the magnetic field's intensity.
- 4. Enhancing Magnetic Fields:** To create a stronger magnetic field, the wire is wound into a coil. Furthermore, adding a ferromagnetic core (like iron) significantly enhances the magnetic field strength, creating an electromagnet.
- 5. Coil Behavior in DC Circuits:** In DC circuits with switching voltages, such as square wave signals, coils introduce a delay in the current reaching its final state—unlike resistors, which respond immediately.
- 6. Energy Storage in Coils:** Coils can store energy in their magnetic field. The energy stored is calculated as $(L * I^2) / 2$, where L is inductance and I is current.
- 7. Output Voltage:** Coils can also be used at the output of switching power supplies (like step-down converters) as energy storage to keep the output voltage at a constant level.

Video 13: Coils / Inductors (Part 2) || Reactance

1. Inductive Reactance (X_L) as Frequency-Dependent

Resistance: The central concept is that inductors oppose changes in current by building and collapsing a magnetic field. This opposition is termed reactance (X_L) and is distinct from standard resistance (R) because power is stored magnetically rather than dissipated as heat.

- 2. Reactive Power and Power Grid Strain:** The build-up and collapse of the magnetic field in inductors lead to power oscillating between the voltage source and the load. This is referred to as reactive power and can strain power grids.
- 3. Phase Shift (Voltage-Current Relationship):** In AC circuits with inductors, the voltage and current waveforms are not perfectly aligned as they are with purely resistive loads. This misalignment is called a phase shift.
- 4. Cheap Inductance Measurement Tool:** A readily available and inexpensive "transistor tester" is recommended as an alternative to RLC meters for measuring inductance.

Video 14: Capacitors

- 1. Introduction:** Capacitors are prevalent in almost all consumer electronics circuits, and their failure can be a common cause of device malfunction. The core function of a capacitor is to store electrical energy in an electrostatic field. This is achieved by separating two conductive plates with non-conductive (dielectric) material. A simple capacitor can be constructed with two parallel conductive plates separated by a small distance.
- 2. Factors Affecting Capacitance:** More space for electrons leads to a bigger electrostatic field, the force on electrons increases, allowing more electrons to accumulate. Dielectric materials, like distilled water, align with the electrostatic field and increase the force on electrons, creating more space for others.
- 3. Polarity (for Electrolytic Capacitors):** Electrolytic capacitors are polarized and must relate to the correct polarity. Reversing polarity can damage them.

- 4. Comparison to Inductors:** Capacitors and inductor coils both introduce reactance in AC circuits; however, capacitors are often preferred for filters because they are typically cheaper and more compact than coils.

Video 15: Temperature Measurement (Part 1) || NTC, PT100, Wheatstone Bridge

- 1. Resistor-based temperature sensors:** Temperature sensors with resistance that change with temperature include NTC thermistors and RTDs such as the PT100.
- 2. Measuring Resistance:** Requires supplying a low constant current (around 1 milliamp) to avoid heating the resistor. Voltage across the resistor is measured, and resistance is calculated using Ohm's Law.
- 3. Circuits to Improve Measurement:** Voltage divider can create offset voltage to cancel the PT100's offset at 0° . Wheatstone Bridge measures the voltage between two identical voltage dividers with one changing resistor value. Differential Op-amp subtracts the offset voltage from the changing PT 100 one.
- 4. Limitations of resistance-based methods:** The concept of thermal inertia is introduced as a common drawback of the discussed resistance-based sensors.

Video 16: Resistors

- 1. Functions:** Resistors are primarily used to limit current flow in a circuit. Multiple resistors in series can be used to divide a supply voltage, creating specific voltage levels for different components. Resistors can facilitate the conversion of data signal voltage levels

between different systems (e.g., Arduino 5V to ESP32/ESP8266 3.3V).

- 2. Types:** Potentiometers are variable resistors, allow for on-the-fly adjustment of output voltage or as input for microcontrollers. Pull-up/Pull-down Resistors are used to define a clear initial state (high or low logic level) for input pins, preventing "floating" inputs and ensuring stable readings.
- 3. Ohm's Law and Current Limiting:** A fundamental application is using Ohm's Law ($V=IR$) to calculate the appropriate resistor value for limiting current to a desired level (e.g., protecting an LED from "immediate DEP").
- 4. Current Sense Resistor Principle:** The current sense resistor principle involves using very small-value resistors to measure current flow. By amplifying the voltage drop across these resistors with a differential circuit and knowing the resistance value, the current can be accurately calculated. This is a key method for current measurement and control.
- 5. Parasitic Effects in AC Circuits:** At higher frequencies, the parasitic inductance and capacitance inherent in a resistor's structure become significant. As capacitive reactance decreases, current flow increases, illustrating the non-ideal behavior of real-world components.

Video 17: Oscillators || RC, LC, Crystal

- 1. Function of Oscillators:** An oscillator's core purpose is to generate periodic alternating voltage signals—such as square, triangle, or sine waves—that function as clock signals for devices or as carrier waves for radio communication and other wireless data exchange. These signals are essential for timing in electronic

systems, including microcontroller processing speeds and multimeter refresh rates.

- 2. Relaxation Oscillators (RC Circuits):** This type of oscillator utilizes the charging and discharging of capacitors through resistors to generate periodic signals. Astable Multivibrator uses "two capacitors C1 and C2 which get charged alternating through a resistor to a certain threshold voltage of the transistor." When a capacitor reaches a threshold, it triggers a transistor to become conductive, discharging that capacitor while the other charges. This alternating charge/discharge cycle creates a "rectangle waveform." 555 Timer IC implements the core idea of charging and discharging a capacitor periodically to create a "stable and variable rectangle wave."
- 3. LC Resonators (LC Tank Circuits):** These circuits, comprising an inductor (L) and a capacitor (C), are used to generate "very high frequencies" and typically produce a sine wave. Oscillation occurs due to the exchange of energy between the capacitor and the inductor. The capacitor stores electrostatic energy when charged, which is then discharged through the inductor, building up stored magnetic energy.
- 4. Crystal Oscillators:** These oscillators offer even greater stability compared to RC and LC types. functions "just like an LC resonator but also uses the mechanical vibrations of a piezoelectric crystal." The piezoelectric crystal vibrates at a very precise frequency when an electric field is applied, and these mechanical vibrations in turn generate an electrical signal.

- 1. Operation:** DC motors utilize direct current to generate rotational movement. They consist of a stationary component called the stator (containing permanent magnets with opposing polarity) and a rotating component called the rotor (containing coils). Commutator and carbon brushes are crucial mechanical components in DC motors. Applying voltage to the coils through the brushes and commutator creates an opposing magnetic field. The interaction between the magnetic fields of the stator magnets and the rotor coils generates a force that pushes and attracts the rotor, causing it to rotate.
- 2. Brushless DC (BLDC) Motor Operation:** The ESC is the electronic component responsible for controlling the speed of BLDC motors. It acts as the electrical equivalent of the mechanical commutator in DC motors. ESCs energize the stator coil pairs in a controlled sequence. By adjusting the frequency of this energizing sequence (which is controlled by an input voltage or signal), the ESC determines the speed of the rotating magnetic field and thus the motor's RPM (Revolutions Per Minute). A higher frequency of energizing steps results in a higher RPM. ESCs utilize arrays of P-channel and N-channel MOSFETs to achieve the required high, low, and floating output states for controlling the coil energizing. The number of parallel MOSFETs in an ESC directly influences its current handling capability, and thus the potential power of the motor it can drive.
- 3. Electronic Speed Controller (ESC):** The ESC is the electronic component responsible for controlling the speed of BLDC motors. It acts as the electrical equivalent of the mechanical commutator in DC motors. ESCs energize the stator coil pairs in a controlled sequence. By adjusting the frequency of this energizing sequence (which is controlled by an input voltage or signal), the ESC

determines the speed of the rotating magnetic field and thus the motor's RPM (Revolutions Per Minute). A higher frequency of energizing steps results in a higher RPM. ESCs utilize arrays of P-channel and N-channel MOSFETs to achieve the required high, low, and floating output states for controlling the coil energizing. The number of parallel MOSFETs in an ESC directly influences its current handling capability, and thus the potential power of the motor it can drive.

- 4. KV Rating:** The KV rating of a BLDC motor represents the theoretical RPM per volt applied. A higher KV rating indicates that the motor will achieve a higher RPM for a given voltage. While voltage is a factor, the ultimate RPM is also limited by the maximum frequency the ESC can achieve, which in turn depends on the characteristics of the motor and the applied voltage. Calculating RPM based on the KV rating and applied voltage provides values that are generally close to reality.

Video 19: I2C and how to use it

- 1. Introduction:** I²C utilizes only two wires for communication: SDA (Serial Data) and SCL (Serial Clock). These connect to specific pins on the master device. I²C operates with at least one master device that initiates and controls the communication, and one or more slave devices that respond to the master's commands. Each slave device on the I²C bus has a unique 7-bit address, which the master uses to identify and communicate with a specific slave. This address is typically found in the slave device's data sheet.
- 2. Communication Sequence (Reading Data):** A typical I²C read sequence follows a similar pattern but with the R/W bit set to 1 and the acknowledge generated by the master after receiving data.

- 3. Data Representation:** While binary representation is the fundamental level, hexadecimal is more commonly used for representing data bytes sent over I²C.
- 4. Practical Application:** An example is provided to demonstrate how to calculate the required data bytes—specifically the PLL value—to tune a TDA5767 FM radio IC to a desired frequency. Using the formula from the datasheet, the calculation is illustrated for tuning to 95.6 MHz.

Video 20: Thyristor, Triac || Phase Angle Control

- 1. Structure & Functionality:** A thyristor has four layers and includes an additional gate terminal. A triac is essentially two thyristors connected in an inverse parallel configuration within a single component. This allows for the control of both the positive and negative half-waves of the AC signal.
- 2. Phase Angle Control Circuit:** The core application demonstrated is a phase angle control circuit, enabling control of power consumption in AC appliances by allowing only a portion of each half-wave to pass through the triac. The circuit works by introducing a controllable delay between the AC signal's zero crossing and the activation of the triac. By varying this delay, the point at which the triac begins to conduct within each half-wave is controlled, thus regulating the amount of power delivered to the load.
- 3. Applications and Disadvantages of Phase Angle Control:** Controls the temperature by regulating the power supplied and adjusts the speed. A significant drawback of phase angle control is the constantly decreasing power factor due to the non-sinusoidal

current waveform created by switching the triac on and off within the AC cycle. This is highlighted as a topic for future discussion.

- 4. Safety Precautions:** Safety is strongly emphasized when working with AC voltages, with a recommendation to avoid direct interaction with high-voltage mains power without proper precautions. An autotransformer is suggested for safely stepping down mains voltage during experimentation.

Video 21: OpAmp (Operational Amplifier)

- 1. Fundamental:** Op amps are depicted as ubiquitous components in electronic circuits, often appearing as triangle-shaped symbols in simplified schematics. They are available as integrated circuits (ICs) in various packages, commonly with multiple op amps per chip.
- 2. Basic Structure:** The core pins of an op amp: the positive input (non-inverting), the negative input (inverting), the output, and power supply pins ($V+$ and ground).
- 3. Golden Rules:** The output attempts to keep the voltage difference between the inputs at zero volts. The input draws no current. This implies infinite input impedance in an ideal op amp. When no feedback is connected, the output will go to either the maximum or minimum output voltage depending on the differential voltage between the inputs. This configuration functions as a comparator.
- 4. Non-Ideal Op Amp Characteristics:** The source acknowledges that real-world op amps are not perfect and have limitations. Key non-ideal characteristics mentioned include: Limited output voltage swing (bounded by supply voltage), Non-infinite input impedance (meaning some input current flows), Non-zero output

impedance (limiting the amount of current that can be drawn),
Limited output current.

- 5. Versatility:** Beyond the specific examples, the source lists numerous other circuits that can be built using op amps, emphasizing their wide range of applications.

Video 22: Transistor (BJT) as a Switch

- 1. Structure and Terminals:** BJTs have three terminals: emitter, collector, and base. The specific function of each terminal in a switching circuit is demonstrated. It is crucial to always check the datasheet for pin configuration as it varies between packages.
- 2. Base Current Controls Collector Current:** The core principle of using a BJT as a switch is that a small current flowing into the base (base current) controls a larger current flowing between the collector and emitter (collector current). This relationship is defined by the current gain (beta or β), a characteristic found in the BJT's datasheet.
- 3. Calculating the Base Resistor:** To ensure the transistor operates reliably as a switch (specifically in the saturated state), the necessary base current needs to be calculated based on the required collector current and the BJT's current gain (using the worst-case value of beta for conservative design). The base resistor value is then determined using Ohm's law, considering the control voltage and the base-emitter forward voltage.
- 4. Disadvantages of BJTs as High-Current Switches:** The biggest disadvantage of BJT's High current switches is the power loss and thus the lower efficiency of the circuits." Power loss occurs due to both the base current and the voltage drop across the collector-

emitter path. This can lead to significant heat generation, requiring thermal management for higher current applications.

- 5. Darlington Transistors for Higher Current Gain:** For switching larger loads or when control signals have limited current capability (like those from a microcontroller), Darlington transistors are beneficial. They consist of two cascaded BJTs, resulting in a much higher overall current gain. This allows a smaller base current to control a significantly larger load current. While providing high current gain, Darlington transistors typically have a bigger collector-emitter and base-emitter voltage drop compared to single BJTs. This can lead to more power loss in certain applications.

Video 23: Transistor (MOSFET) as a Switch

- 1. Efficiency:** The MOSFET only has an energy loss of 0.6 watts across as equivalent collector emitter path and thus increases the overall efficiency of the circuits up to 97%. This means the significant efficiency advantage of MOSFETs over BJTs for switching higher power loads.
- 2. Voltage Control:** Unlike BJTs, which rely on base current to switch loads, MOSFETs require only sufficiently high voltage at the gate with virtually no current. This fundamental difference is key to understanding how the two types of transistors operate.
- 3. Linear Region Operation:** When used as a switch, MOSFETs operate in the "linear region in which the resistance of the drain to source path is almost constant," leading to low voltage drop and power dissipation.
- 4. Voltage Oscillations with Inductive Loads:** Switching inductive loads can cause a damped oscillation that reaches peaks around 64

volts when the MOSFET switches off. This is a critical issue to address for MOSFET longevity.

5. **Switching Losses at High Frequencies:** Switching Losses at High Frequencies: "With a frequency of 1MHz we have switching losses of 80mW." While gate losses are negligible at low frequencies, they become significant at higher frequencies.

Video 24: Stepper Motors and how to use them:

1. **Introduction:** Stepper motors are preferred for positioning applications like 3D printers due to their ability to precisely control rotational movement in discrete steps and their inherent holding torque.
2. **Structure:** Contains four permanent magnets with alternating polarity (North and South). Each pole shoe has 50 teeth, with an offset between the teeth of different pole shoes. This creates alternating North/South magnetized teeth when viewed from the front. Also possess teeth that are not initially magnetized. It contains eight physically separated coils, wired as two pairs of coils.
3. **Mechanism:** Powering specific coil pairs generates magnetic poles in the stator teeth, attracting the rotor's permanent magnet teeth. Sequentially activating the coil pairs in a defined each step shifts the magnetic field by 45 degrees, causing the rotor to move one tooth position. Four-step order causes the rotor to move in precise increments.
4. **Step Angle and Steps Per Rotation:** The motor described has 50 teeth and requires four steps to move one tooth to the location of the next. This results in 200 steps per rotation (50 teeth * 4 steps). The step angle is calculated as $360^\circ / 200 \text{ steps} = 1.8^\circ$. Stepper

motors require drivers to easily control their current direction through the coils. An H-bridge circuit allows current flow in either direction. The source builds a basic driver using MOSFETs and an Arduino. A significant advantage of stepper motors is their ability to maintain their position when current flows through the coils, even without rotation.

- 5. Microstepping Drivers (ICs):** Implementing microstepping effectively requires a constant current driver that can vary the current strength. Specialized Integrated Circuits (ICs) like the A4988 are designed for this purpose and are basically more advanced H-bridges.

Video 25: Servos and how to use them

- 1. Characteristics:** Common servos have a sawtooth shaft, three wires (Brown: Ground, Red: VCC (4.8-7.2V), Orange: Control Signal), and are typically controlled by a PWM signal.
- 2. Position Mapping to PWM:** A 1ms on time corresponds to -90° , 1.5ms to 0° , and 2ms to $+90^\circ$, allowing for a 180° rotation range.
- 3. Internal Components:** Servos contain reduction gears (decreasing RPM and increasing torque), a DC motor, a potentiometer for position feedback, and a control IC (like the KC 5188) with an H-bridge to drive the motor.
- 4. Control Mechanism:** The control IC compares the potentiometer's voltage (current position) to the target position indicated by the PWM signal and adjusts the motor's rotation until the difference is zero. An Arduino with the servo library can easily generate the required PWM signal, although the full 180° range may require a signal varying between 0.5ms and 2.5ms, which the library supports. A 555 timer IC with external components can also

generate a suitable PWM signal for servo control, even if the periodic time isn't perfectly constant.

- 5. Pre-made Continuous Rotation Servos:** Servos with these modifications pre-installed are available, sometimes offering additional control over the simulated 0° position.

Video 26: **555 Timer IC**

- 1. Utility:** The 555 timer IC is highlighted as an incredibly popular and useful component in building electrical circuits, making our life easier.
- 2. Internal Structure and Pinout:** Three 5 Kiloohm resistors in series, which gives the IC its name and creates a voltage divider, two comparators, an integrated flip-flop, an output driver, a bipolar junction transistor at the discharge pin. Pin 1 is connected to the ground. Pin 2 (Trigger) is directly connected to the negative input of the first comparator. Pin 3 (Output) is connected to an output driver and the flip-flop's output. Pin 4 (Reset) is directly connected to the reset pin of the flip-flop and can be used to instantly reset the flip-flop by connecting it to ground. Pin 5 (Control Voltage) connects to the negative input of the second comparator and the voltage divider. Pin 6 (Threshold) connects to the positive input of the second comparator. This pin monitors the voltage of an external capacitor in timing circuits. Pin 7 (Discharge) directly connected to the collector of a bipolar junction transistor, which is used to discharge an external capacitor. Pin 8 (VCC/Supply Voltage) is connected to the supply voltage.
- 3. Basic Circuit Configurations:** Generates a single, temporary output pulse of a defined duration when triggered. The high output state is unstable, while the low state is stable. The pulse duration is

set by external resistor and capacitor values. It is commonly used to create delays for notification lights. Creates two stable output states (high and low) and acts as a simple latch or flip-flop. It does not require RC components and uses the Trigger (Pin 2) as the set pin and Reset (Pin 4) as the reset pin. Applying a ground potential to either pin 2 or pin 4 toggles the output state. Perfect for turning LEDs on and off manually with push buttons.

4. **Advantages of CMOS 555 Timers:** By using diodes and a potentiometer, the charging and discharging currents can be separated and adjusted, allowing for the creation of a beautiful PWM signal with constant frequency.

Video 27: ADC (Analog to Digital Converter)

1. **Sampling Rate:** This refers to how frequently the ADC takes a measurement of the analog signal. A higher sampling rate captures more data points and allows for a more accurate representation of a rapidly changing signal. The source uses the example of a 10 kHz sine wave and demonstrates that a low sampling rate results in "complete bullshit" when trying to recreate the function.
2. **Resolution:** This refers to the number of bits the ADC uses to represent the analog voltage. A higher resolution means the ADC can distinguish between smaller voltage differences, resulting in a more precise digital value.
3. **Successive Approximation ADCs (SAR ADCs) Work:** This circuit captures the analog voltage at a specific point in time and holds it steady for the duration of the conversion. This is achieved using a capacitor and a voltage follower. This component compares the sampled analog voltage with a voltage generated by DAC.

4. Alternative ADC Type: Flash ADCs: particularly suitable for DIY projects as they do not require a DAC. A Flash ADC "basically consists of four comparators and five resistors" (for a 2-bit version) and uses a resistance network to create different voltage references for each comparator. The input voltage is compared to these references, and the comparator outputs are fed into an encoder with a truth table to produce the digital value. While "ridiculously fast", Flash ADCs "usually have a low resolution" due to the exponential increase in the number of comparators needed for higher resolutions.

Video 28: **IGBT and when to use them**

- 1. Comparison of IGBTs and MOSFETs as power switches:** The core focus is to differentiate between BJTs and MOSFETs and identify their appropriate use cases based on their distinct operating principles and characteristics.
- 2. Internal Structure of IGBTs:** Understanding how IGBTs are constructed from elements of both MOSFETs and BJTs.
- 3. Switching Characteristics:** Analyzing the differences in switching speed and behavior between IGBTs and MOSFETs.
- 4. Power Loss Characteristics:** Comparing the power dissipation of IGBTs and MOSFETs under load.
- 5. Suitable Applications:** Identifying the conditions under which an IGBT is a better choice than a MOSFET.
- 6. Driving IGBTs:** Discussing the methods and requirements for controlling the gate of an IGBT.

Video 29: **Solar Panel & Charge Controller:**

- 1. Regenerative Energy Sources:** Solar panels are identified as an easy-to-use, regenerative energy source that converts light into electricity, suitable for powering loads or charging batteries. Solar panels are composed of individual "solar cells." These cells are the fundamental unit that generates voltage when exposed to light.
- 2. Voltage Generation and Series Connection:** A single solar cell generates a low voltage (around 0.5 volts). To achieve higher output voltages suitable for practical applications, many solar cells are connected in series within a solar panel. For example, a 100-watt panel discussed connects "36 cells in series to create an open circuit voltage of around 14 point 3 volts."
- 3. Challenges of Series Connections:** Partial Shading: A significant drawback of series connections is the impact of partial shading. If even a small portion of the panel is shaded, the affected cells act as a higher resistance, drastically reducing the overall power output.
- 4. Bypass Diodes:** Bypass diodes are added in parallel to solar cells (or groups of cells) to address the issue of partial shading. These diodes allow current to flow around a shaded cell.
- 5. Power Output Under Varying Loads:** The actual power output of a solar panel varies depending on the connected load.
- 6. Maximum Power Point Tracking (MPPT) Controllers:** MPPT controllers are the best ones of this kind. They utilize switching converters to act as the ideal MPP loads and thus a charge of the battery. MPPT controllers constantly track and adjust the load presented to the solar panel to ensure it operates at its MPP, maximizing the energy harvested.
- 7. Pulse Width Modulation (PWM) Controllers:** Other, less efficient charge controllers, such as PWM controllers, simply use PWM to charge the battery but they do not try to find the MPP and thus can decrease the efficiency of up to 40%.

Video 30: Microcontroller (Arduino) Timers

- 1. Precise Timing:** Examples such as alarm clocks, LED matrix animations, and audio generation are highlighted to demonstrate the importance of accurate timing in electronic applications.
- 2. Limitations of delay ():** While simple, the delay () function in Arduino sketches is inefficient and can block the main program loop, preventing the microcontroller from responding to other inputs or tasks. It also suffers from potential timing inaccuracies over longer durations.
- 3. Timers as Dedicated Peripherals:** Microcontrollers, including the ATmega328P on the Arduino Uno, feature dedicated hardware timers that can handle precise timing independently of the main program execution. These timers are set up once and then run continuously in the background.
- 4. Timer Modes and Functionality: Timers offer various modes of operation to achieve different timing goals:**
- 5. Normal Mode:** The timer counts to a maximum value (overflow) and then resets. Overflow flags and associated interruptions can be used to trigger events.
- 6. CTC Mode (Clear Timer on Compare Match):** The timer counts to a specific value defined in a "compare register." When the counter matches this value, a match flag and interruption are triggered. This allows for more precise timing intervals than relying solely on overflows and enables multiple independent timing events.
- 7. PWM Modes (Pulse Width Modulation):** Timers can be configured to generate PWM signals, which are essential for controlling motor speed, LED brightness, and generating the duty cycle and frequency of the PWM signal can be adjusted.

Video 31: Schottky Diode & Zener Diode

1. **Common Diode Review:** the fundamental behavior of a common diode:

Forward Bias: When a positive voltage is applied to the anode and a negative voltage to the cathode, current flows. This creates a characteristic forward voltage drop.

Reverse Bias: When the voltage potential is reversed (positive at cathode, negative at anode), no current flows.

2. **Schottky Diode:** The Schottky diode is introduced as a popular alternative with distinct advantages, primarily due to its construction using a metal-semiconductor junction rather than a semiconductor-semiconductor junction like common diodes. A demonstration compares the 1N4007 diode, which shows a 0.87V drop and 0.87W loss at 1A, with the 1N5819 Schottky diode, which shows only a 0.45V drop and 0.45W loss under the same conditions. This results in significantly lower power loss and heat generation—around 50°C for the Schottky—making it highly effective for reverse voltage protection and improving overall circuit efficiency.
3. **Zener Diode:** The Zener diode, also known as the 'Z' diode, is presented with a focus on its unique behavior when operated in reverse bias. While a Zener diode can be used like a common diode in forward bias, resulting in a comparable high voltage drop. The primary function of a Zener diode is realized when connected reverse biased, which means that the cathode has positive potential and the Anode the negative potential.

Video 32: Relays & Optocouplers

- 1. Function:** Relays are described as electromechanical switches that use electromagnetic principles to open or close an independent circuit. By applying voltage to the pins of the coil, current will flow through it which thus creates a magnetic field that attracts the anchor on top of the coil and therefore closes the previously open contacts. This allows a low-voltage control signal to switch a potentially high-voltage load. Specified voltage and current limitations for both the coil and the switch contacts, which can be found on the component or in its data sheet. Applying too low a voltage to the coil can result in unreliable activation, while too high a voltage can damage the coil due to excessive heat and overcurrent.
- 2. Safety Feature (Flyback Diode):** When the coil of a relay is de-energized, the collapsing magnetic field can induce a significant voltage spike. This can damage sensitive control circuitry like transistors. The solution is to add a flyback diode parallel to the coil, allowing the induced current to flow and prevent the overvoltage.
- 3. Identification:** Relays are often identifiable by their clicking sound when activating and deactivating. Important information like coil voltage is typically printed on the enclosure.

Video 33: **Strain Gauge/Load Cell and how to use them to measure weight**

- 1. Strain Gauge Principle:** The core concept of measuring force/weight by detecting changes in the electrical resistance of a strained material.
- 2. Wheatstone Bridge Configuration:** The necessity of using a Wheatstone bridge to effectively measure the small resistance

changes in a strain gauge by converting them into a measurable voltage difference.

- 3. Temperature Compensation:** The challenge of temperature sensitivity in strain gauges and how to mitigate it using half or full bridge configurations.
- 4. Load Cells as Integrated Solutions:** Load cells are presented as a simpler alternative to individual strain gauges, offering a pre-built Wheatstone bridge within a mechanical structure.
- 5. Signal Amplification and Analog-to-Digital Conversion (ADC):** The need to amplify the small voltage output from a Wheatstone bridge and convert it into a digital signal for processing by a microcontroller.
- 6. High-Resolution ADC Solutions:** The benefits of using specialized breakout boards like the HX711 with integrated amplifiers and high-resolution ADCs for more sensitive measurements.

Video 34: Schmitt Trigger and when to use them

- 1. Introduction:** Schmitt triggers are introduced as a solution to the noise-related oscillation problem seen with basic comparators. They are created by adding a couple of resistors to a comparator. The output is pulled high *only* if the monitored voltage passes the high threshold. This creates a hysteresis voltage between the two thresholds where no switching of the output is possible.
- 2. Types:**
 - Non-inverting Schmitt Trigger:** The output state follows the relationship described above (output high when voltage passes high threshold, output low when voltage goes below low threshold).
 - Inverting Schmitt Trigger:** Works similarly to the non-inverting

type but reverses the output state for its high and low threshold values.

3. Implementation and Characteristics: While Schmitt triggers can be built with op-amps and resistors, the source focuses on using dedicated Schmitt trigger ICs, specifically mentioning the 74HC14 hex inverting Schmitt trigger IC. The 74HC14 contains six inverting Schmitt triggers. The threshold voltages for a specific IC can be found in its datasheet. In the example given, the threshold voltages for the 74HC14 were found to be around 2.1 volts and 3.1 volts, correlating with the datasheet.

Video 35: SPI and how to use it

- 1. Introduction to SPI:** The Serial Peripheral Interface (SPI) protocol is an alternative to I2C, highlighting its structure with a master device communicating with one or more slave devices.
- 2. Interfacing with a DS3244 RTC:** The core example used throughout the excerpt is the connection and programming of a DS3234 RTC IC with an Arduino using SPI. This serves as a practical demonstration of the protocol's application.
- 3. SPI Pin Configuration and Functionality:** A detailed explanation of the essential SPI pins (CLK, MOSI, MISO, and SS/CS) and their roles in data transmission is provided.
- 4. SPI Modes and Data Handling:** The concept of SPI data modes (Mode 0, 1, 2, and 3) is introduced, explaining how data is read relative to the clock signal's edge and polarity.
- 5. Comparison with I2C:** A brief comparison between SPI and I2C is made, highlighting the limitations and advantages of SPI, particularly its speed advantage.

Video 36: What is Impedance? (AC Resistance?)

- 1. Impedance is the AC equivalent of resistance:** While resistors have a straightforward effect in DC circuits, inductors and capacitors behave differently when subjected to alternating current (AC). Impedance combines the effects of resistance, inductance, and capacitance on AC circuits.
- 2. Inductors and capacitors have significant influence on AC current flow:** Unlike in DC circuits where they primarily act as energy storage, inductors and capacitors actively resist the flow of AC current. This "resistance" is known as reactance.
- 3. Reactance is frequency dependent:** The amount of reactance offered by an inductor or capacitor changes with the frequency of the applied AC voltage.
- 4. Resistors, inductors, and capacitors impact both the magnitude and phase of AC current:** Resistors only affect the magnitude of the current, while inductors and capacitors also introduce a phase shift between the voltage and current waveforms.
- 5. Complex numbers are necessary to represent impedance:** Combining the effects of resistance (real) and reactance (imaginary) requires the use of complex numbers to accurately represent impedance and perform calculations in AC circuits.

Video 37: True, Reactive, Apparent & Deformed Power

- 1. Apparent Power:** Apparent power (measured in Volt-Amperes, VA) is introduced as the total power being drawn, calculated by simply multiplying voltage and current.

- 2. True Power:** True power (measured in Watts, W) is defined as the power that performs useful work, such as heating a resistor or moving an electric motor.
- 3. Reactive Power:** Reactive power (measured in Volt-Ampere Reactive, VAR) is power that oscillates between the source and the load, being stored and then released. It is associated with components like inductors and capacitors and is characterized by a phase shift between voltage and current.
- 4. Power Factor:** The power factor is defined as the relationship between true power and apparent power. "Now the power factor describes the relation between true power and apparent power". For loads where reactive power is only due to phase shifts from inductors and capacitors, the power factor is equal to the cosine of the phase angle between voltage and current (cosine Φ). This explains why AC motors are often rated with a cosine Φ .
- 5. The Power Triangle:** True power, reactive power, and apparent power form a right triangle in a complex plane. True power is on the real axis, reactive power is on the imaginary axis (upwards for inductive, downwards for capacitive), and apparent power is the resulting vector.

Video 38: Controlling a BIG LED Matrix?! How Shift Registers work!

- 1. Reverse Engineering and Understanding Complex Electronic Systems:** There is the process of examining a custom-made LED matrix PCB to understand its internal connections and components.
- 2. Utilizing Shift Registers (Serial-In, Parallel-Out):** A core theme is the application and functionality of SIPO shift registers (specifically the stp16cp05) to control many LEDs using a limited number of microcontroller pins.

- 3. Multiplexing for Efficient LED Control:** The video explains and demonstrates the concept of multiplexing as a method to control rows or segments of LEDs sequentially, creating the illusion of a static display.
- 4. Microcontroller Implementation:** There are described how an Arduino Nano is used to generate the necessary control signals (serial data, clock, latch) to drive the shift registers and implement multiplexing.
- 5. Challenges in Programming Large Matrix Displays:** The video highlights that controlling a large matrix requires careful programming, including timing and data management.

Video 39: How safe is contactless payment? || How does RFID & NFC work?

- 1. Contactless payment prevalence:** The increasing use of contactless payment methods like Google Pay and contactless cards.
- 2. Underlying technology:** The reliance of contactless payment on Radio Frequency IDentification (RFID) and Near Field Communication (NFC) technologies.
- 3. Mechanism of RFID:** How RFID readers and tags communicate wirelessly through magnetic fields and modulated signals.
- 4. Distinction between RFID and NFC:** While NFC is a type of RFID, it involves more standardized rules, uses high frequency (13.56 MHz) exclusively, requires closer proximity, and allows for more complex data exchange including reader-to-reader communication.
- 5. Security of contactless payment:** Examining the potential risks and built-in safety measures.

- 6. Practical application of RFID:** Demonstrating simple RFID projects with Arduino and various reader ICs (RDM6300, PN532, RC522).
- 7. Challenges in reading payment cards:** Difficulty in easily reading data from modern payment cards using standard RFID/NFC reader modules.

Video 40: **Does a DIY Audio Crossover make sense? How passive filters work**

- 1. The Role of Audio Crossovers:** Audio crossovers are essential for separating a full-range audio signal into specific frequency bands suitable for different loudspeaker drivers (woofers and tweeters).
- 2. Passive Filter Components:** Resistors, capacitors, and inductors are the fundamental building blocks of passive audio crossovers, each with unique frequency-dependent properties.
- 3. Filter Types and Order:** Combining these components creates different filter types (low-pass, high-pass) and varying "orders," which determine the steepness of the frequency damping. Higher-order filters provide quicker removal of unwanted frequencies.
- 4. Cutoff Frequency:** A critical parameter for filters, the cutoff frequency represents the point at which the signal is attenuated by -3 dB (approximately 0.707 times the input voltage).
- 5. Importance of Loudspeaker Matching:** A commercially designed audio crossover is precisely tuned to the specific frequency response of the accompanying loudspeaker drivers, making a simple replacement or generic DIY approach problematic for optimal sound quality.
- 6. DIY Feasibility (with Caveats):** While theoretically possible to design a DIY crossover, it is complex and requires specialized

tools (like simulation software) and knowledge of the loudspeaker's characteristics to be effective.

Video 41: Is it easy to create your own Transformer? Everything you need to know about Transformers!

- 1. Introduction and Function:** Transformers are typically used when plugging devices into outlets, like charging phones or powering laptops. They transform high mains AC voltage into lower AC voltage for safe device use.
- 2. Video Purpose and Sponsorship:** The video explains how transformers work and explores the ease of creating one. It is sponsored by Jael CPCB, offering PCB services like file upload and fast delivery.
- 3. Basic Structure:** Transformers consist of a metal core made of electrical steel sheets and two coils wrapped around it. A simplified diagram shows a primary (mains voltage) and secondary (low voltage) coil.
- 4. Working Principle (No Load):** Applying mains voltage to the primary coil (high resistance) creates a magnetic flux that flows through the core to the secondary coil. This changing flux induces the output voltage in the secondary coil according to the induction law.
- 5. Working Principle (With Load):** Connecting a load to the secondary coil causes secondary current to create a flux that impacts both coils. This allows more current flow on the primary side to match the load.
- 6. Losses and Efficiency:** Without a load, transformers have real power losses mainly from iron losses (eddy currents and

hysteresis). Iron cores are made with laminated sheets to reduce eddy currents.

- 7. Improving Power Handling:** Increasing the iron core's cross-section area allows transformers to handle more power. Increasing the operating frequency also allows smaller cores, as seen in switch-mode power supplies.
- 8. Frequency and Core Material:** Higher frequencies increase iron losses, leading to the use of less conductive ferrite materials in high-frequency applications. Ferrites have lower maximum magnetic flux density compared to electrical steel sheets.
- 9. Leakage Flux:** High leakage flux can substantially lower a transformer's output voltage. High magnetic permeability cores (iron or ferrite) are used to force flux through the core and minimize leakage.

Video 42: **Controlling Mechanical 7-Segment Displays?! How RS-485 and UART work!**

- 1. Mechanical 7-Segment Displays:** These displays use small pieces of white plastic and magnets instead of LEDs to show segments. Each segment has a magnet controlled by electromagnets, reversing polarity with 12V DC to move the plastic piece.
- 2. Display Control and Power:** The electromagnets keep their magnetic polarity even without current flowing, meaning the displayed number stays without requiring continuous electrical energy. Controlling multiple displays requires many microcontroller pins or a more complex circuit and code, which can be time-consuming.
- 3. Alfa Zeta Module and Circuit:** The company Alfa Zeta, producer of the displays, sent a large module with a control circuit. The

video explores how this circuit works and how to control it using Arduino UART and RS-485 for a YouTube subscriber counter.

4. **Examining the Control Circuit:** The control circuit was removed from the display PCB for examination and initially seemed complex due to the number of ICs. Reverse-engineering involved finding datasheets and using a multimeter to trace connections.
5. **Circuit Components and Operation:** The ATmega32A microcontroller heads the operation, controlling electromagnets via high-voltage source drivers and Darlington transistor arrays. The suspected control method is multiplexing, where a source IC powers one display at a time while transistors activate specific segments.
6. **Theory and Communication Question:** Practical testing showing displays changing numbers one-by-one supported the multiplexing theory. The next step was to figure out how to communicate a desired number to the microcontroller.
7. **Communication Interface on PCB:** The PCB includes two RJ11 connectors which, according to the manufacturer, use a specific pinout for communication. This communication interface utilizes RS485 standard.
8. **Understanding RS485:** RS485, also known as TIA485 or EIA485, is an industry standard for asynchronous serial data transfer. Unlike synchronous protocols like SPI or I2C which use a clock line, RS485 relies only on data lines for communication.

Video 43: **Improving my electric longboard with a CAN Bus! What can the CAN Bus do**

1. **Solving an Electric Longboard Performance Issue:** The primary motivation for implementing the CAN bus is to address the issue

of inconsistent motor startup times in dual-motor electric longboards when using small input signals.

2. **Introduction to the CAN Bus:** The source provides a clear and concise explanation of what the CAN bus is, its purpose, and its primary application in automotive systems.
3. **Technical Details of the CAN Bus:** The video delves into the electrical characteristics, communication protocol, and key features of the CAN bus, such as dominant/recessive bits and the ID-based priority system.
4. **Practical Implementation:** The source demonstrates the practical steps involved in connecting and configuring the CAN bus on FSEC electronic speed controllers (ESCs).
5. **Benefits of Using the CAN Bus:** The video highlights the advantages of using a CAN bus, including improved motor synchronization and the potential for implementing features like traction control.
6. **Comparison to Other Data Transmission Methods:** The source briefly compares the CAN bus to the RS-485 data transmission protocol, noting similarities in its half-duplex and asynchronous nature, and the requirement for termination resistance.

Video 44: **Building a Digital Music Player with I2S?! What is I2S!**

1. The ESP32's internal DAC has a limited 8-bit resolution, making it unsuitable for playing 16-bit audio files without significant quality loss.
2. I2S (Inter-IC Sound) is a dedicated electrical serial bus interface specifically designed for digital audio communication between integrated circuits.
3. I2S communicates PCM (Pulse-Code Modulation) audio data.

4. The three primary I2S pins are Word Select (WS), Serial Clock (SCK), and Serial Data (SD). These pins may have slightly different names on different breakout boards.
5. The Word Select line indicates the left and right channels for stereo audio transmission.
6. The Serial Clock is used to sample the data on the Serial Data line at its rising edge.
7. The frequency of the Serial Clock in I2S is adjustable and depends on the sampling rate, bit resolution, and whether the audio is mono or stereo.
8. The ESP32 microcontroller has built-in I2S peripherals with selectable pins, allowing for flexible wiring.
9. Implementing I2S communication with the ESP32, while requiring specific code, can be simplified with existing libraries.
10. Using an I2S amplifier board (like the MAX98357A) is a practical method for achieving high-quality audio output from an ESP32 with 16-bit audio files.
11. I2S is also useful for digital audio input, as demonstrated with the I2S microphone (INMP441).

Video 45: Does this old Induction Motor still work? || How do Asynchronous Motors work?

1. **Introduction to Asynchronous Motors:** The video introduces asynchronous motors (also known as induction motors) as a widely used motor type, highlighting their difference in size and complexity compared to common hobbyist motors like stepper, DC, or BLDC motors.
2. **Basic Operation and Construction:** The core of the video explains how asynchronous motors work, focusing on the

interaction between a rotating magnetic field in the stator and induced currents in the rotor. It details the key components: the stator (containing coils) and the rotor (typically a squirrel cage).

- 3. Electrical Connections and Configurations:** The video demonstrates how to connect a three-phase asynchronous motor, explaining the significance of star and delta configurations and their relationship to the applied voltage (230V/400V).
- 4. Generating a Rotating Magnetic Field:** The source emphasizes that asynchronous motors do not rely on permanent magnets. Instead, the rotating magnetic field is generated by applying three-phase AC voltage to the stator coils, which are positioned 120 degrees out of phase.
- 5. The Role of the Rotor and Induction:** The rotating magnetic field in the stator induces a voltage and subsequent current in the conductive bars of the squirrel cage rotor. This induced current creates a magnetic field in the rotor that opposes the stator's field, resulting in torque and rotation.
- 6. Asynchronous Operation and Slip:** A crucial concept is that the rotor rotates slightly slower than the stator's rotating magnetic field. This difference in speed, known as "slip," is essential for voltage to be induced in the rotor. This characteristic is the origin of the term "asynchronous."
- 7. Single-Phase Asynchronous Motors:** The video briefly touches upon how single-phase asynchronous motors work, explaining the use of a capacitor to create a phase shift that approximates a rotating magnetic field, suitable for smaller applications.

Video 46: Building a Tube Amp! Does it produce better audio quality though?

- 1. Historical Context of Vacuum Tubes:** The video begins by placing vacuum tubes in historical context, noting their invention in 1906 and their subsequent replacement by transistors (first created in 1947). Despite being considered "a relic of the past," they are still used in modern audio equipment, prompting the question of their continued relevance.
- 2. Investigation of a Commercial Tube Amplifier:** The author purchases and examines an 80€ tube amplifier. The product is praised for its build quality, easily replaceable tubes, and multiple input/output options (wired stereo, Bluetooth, speakers, headphones).
- 3. Vacuum Tubes as Pre-amplifiers:** Disassembly of the purchased amplifier reveals that the vacuum tubes are used for *pre-amplification* only. The main power amplification is handled by other integrated circuits (operational amplifiers, headphone amplifier, and a Class D amplifier).
- 4. Functionality of a Triode Vacuum Tube:** The video provides a basic explanation of how a triode vacuum tube works. Key pins discussed are the plate (anode), cathode, grid, and heater. Current flows from the cathode to the anode when the heater excites electrons.
- 5. Distortion and Perceived Audio Quality:** The video delves into the concept of distortion and how it relates to the perceived sound of tube amplifiers. While transistor characteristics curves are generally more linear, vacuum tube curves show "noticeably more curves," indicating they will produce more distortions.
- 6. Conclusion on Building a Full Tube Amplifier:** Based on the investigation, including the high voltage requirements, heat generation, and the subjective nature of the perceived audio

benefit, the author concludes that they have "pretty much no interest in creating my own proper tube amplifier system.

Video 47: The Best Protection for your Circuits? eFuse! Here is why they are awesome!

- 1. The Importance of Circuit Protection:** The source emphasizes the crucial need for protection circuits when powering electronic projects, particularly when utilizing various power sources beyond simple USB connections. It highlights the potential for damage to circuits and power sources due to common errors and external factors.
- 2. Limitations of Simple Powering Methods:** While recommending USB power banks for portability and their built-in protection, the author notes that for projects powered by other sources (batteries, solar panels), dedicated protection is essential.
- 3. eFuse as a Comprehensive Solution:** The central theme is the eFuse IC as a versatile and effective solution for providing multiple essential protection features within a single component.
- 4. Practical Implementation and Demonstration:** The source provides a practical guide to selecting and implementing an eFuse IC (specifically the TPS259621) for protecting a simple Arduino circuit, demonstrating how to set specific protection parameters using external components.

Video 48: Everything you need to know when buying/using an Oscilloscope!

- 1. Function of an Oscilloscope:** Visualizing voltage and/or current over time. Essential for analyzing waveforms in modern

electronics, especially switched mode power supplies and digital communication.

- 2. Oscilloscope Selection:** Key parameters to consider when choosing an oscilloscope for specific needs (channels, bandwidth, sampling rate).
- 3. Basic Oscilloscope Operation:** Connecting probes, understanding scaling factors (x1, x10), proper triggering, vertical and horizontal divisions, and using measurement features/cursors.
- 4. Advanced Techniques:** AC coupling for ripple measurement, single shot capturing, current measurement methods, and safe mains voltage measurement.
- 5. Safety Precautions:** Emphasizing the dangers of incorrect mains voltage measurement and the importance of using appropriate probes or techniques.

Video 49: **Probably the most used component nobody knows of!** **TL431 Guide!**

- 1. Importance of Switched-Mode Power Supplies (SMPS):** The source begins by acknowledging the ubiquity and efficiency of SMPS in modern electronics.
- 2. Introduction of the TL431:** The core focus is the TL431 IC, which the author discovered while building a DIY SMPS. Initially unfamiliar with the component, the author's research revealed its widespread applications.
- 3. Internal Structure and Basic Operation:** The simplified schematic of the TL431 resembles a Zener diode with a reference voltage pin. The functional block diagram reveals the IC consists of a "comparator, a transistor, a diode and a voltage reference which is typically 2.495V. The IC requires a power voltage at the

cathode between the internal reference voltage and 36V, drawing a maximum of around 1mA. The pinout consists of "ref, anode and cathode."

- 4. Adjustable Zener Diode Functionality:** By adding a voltage divider between the cathode, ref pin, and anode, the TL431 can be configured as an adjustable Zener diode. The threshold voltage can be set using a simplified formula based on the 2.5V internal reference and the resistor values in the voltage divider.
- 5. Versatility in Circuits:** The core principle of the TL431 – its ability to "monitor a voltage and switch at a certain threshold" – makes it ideal for both monitoring and feedback circuits.

Video 50: This component can control tons of circuits! Digital Potentiometer Guide!

- 1. Limitations of Mechanical Potentiometers:** The primary motivation for using digital potentiometers is the inability to dynamically control the resistance of a mechanical potentiometer with a microcontroller or other digital means. Mechanical potentiometers require manual adjustment.
- 2. Introduction to Digital Potentiometers:** These integrated circuits (ICs) provide a digitally controlled alternative to traditional potentiometers, allowing for automated adjustment of resistance.
- 3. Functionality of Digital Potentiometers:** Digital potentiometers mimic the behavior of mechanical potentiometers, typically consisting of a series of resistors with digitally controlled switches that select a tap point (wiper). This allows them to function as either a variable resistor or a voltage divider.

- 4. Communication Interfaces:** Digital potentiometers utilize various communication protocols to receive instructions, with I2C and SPI being common, although simpler 3-pin digital input options exist.
- 5. Resolution:** A key difference from mechanical potentiometers is that digital potentiometers have a finite number of steps (wiper positions), limiting the resolution of the resolution or voltage division.
- 6. Voltage and Current Limitations:** Digital potentiometers have specific voltage and current limits that must be respected to avoid damaging the IC. These limits can vary significantly between different models.
- 7. Practical Applications:** Digital potentiometers can be used in various circuits where variable resistance or voltage division is required, such as dimming LEDs, setting sensor thresholds, or adjusting output voltages in power converters.
- 8. Importance of Datasheets:** Understanding the specifications, pinout, communication protocol, and limits outlined in the digital potentiometer's datasheet is crucial for successful implementation.

Video 51: Negative Voltages are more important than you think! So here is how to make them!

- 1. Single vs. Dual Rail Power Supplies:** Standard power supplies typically provide a single positive DC output voltage relative to ground (GND). Dual rail power supplies provide both positive and negative DC output voltage relative to a common ground.
- 2. Commercial Dual Voltage Boards:** Pre-built modules are available that easily convert a positive input voltage into both positive and negative output voltages. After hooking their input up

to a voltage of 5V we can measure an output voltage of +12V between V+ and GND and -12V between GND and V-.

- 3. Inverting Charge Pump from a Boost Converter:** This method utilizes a common boost converter circuit and adds an "inverting charge pump" circuit to generate a negative voltage. It is called an inverting charge pump, and it works by firstly applying a high frequency square wave voltage to the first capacitor that gets kindly provided by the boost converter.
- 4. Center Tapped Transformer:** This method, often used in more robust power supplies, utilizes a center tapped transformer to generate both positive and negative AC waveforms relative to the center tap (which serves as GND). These waveforms are then rectified and smoothed to create stable DC voltage rails.
- 5. Alternative:** Two identical output winding transformers can be connected to function as a center tapped transformer.
- 6. Voltage Divider with Operational Amplifier Buffer:** To improve the stability of the virtual GND in the resistive divider method, an operational amplifier can be used as a buffer. To improve this though we can add an operational amplifier as a buffer between the voltage divider and the virtual GND.

Video 52: **Mechanical Switches are Obsolete?! Switch to a Latch Circuit!**

- 1. Latch Circuit Definition:** A latch circuit turns a switching element on or off and keeps it in that state. It is triggered by a small voltage pulse on set and reset inputs.
- 2. Latch Circuits Applications:** They are commonly used in corridor lighting, power supply buttons, and overcurrent protection circuits.

They are mandatory for circuits where rapid switching is undesirable, such as self-deactivating microcontrollers.

3. Comparison with Mechanical Switches: Latch circuits offer pros and cons compared to classic mechanical toggle switches used for lighting and power switches. For certain electronic circuits, latch circuits are a mandatory choice.
4. Implementing Latches with ICs: You can start with dedicated SR Latch ICs like the 74LS279, which have set (S) and reset (R) inputs and a Q output. Applying a high voltage (1) to set the output high, while applying high to reset turns it low.
5. Basic Latch Structure (Logic Gates): The simplest SR Latches consist of two NOR gates connected. Logic gates like NOR, OR, AND, and NOT have outputs based on a truth table of their inputs.
6. Building Latches with Components: Building digital logic circuits like latches with transistors, resistors, and capacitors is often cheaper than using dedicated ICs. This component-based approach can also offer higher current capabilities and the ability to add extra features.
7. Toggle On/Off Latch Circuit (Component-Based): A toggle latch can be built using a P-Channel MOSFET and NPN BJTs. Pushing a button activates a BJT that pulls the MOSFET gate low, turning on the load, and a capacitor helps manage the switching timing.
8. Set/Reset Latch Circuit (Component-Based): A similar circuit uses BJTs and a MOSFET for set and reset functionality. A set pulse turns on the circuit by activating a BJT and MOSFET, while a reset pulse turns it off by activating another BJT to pull the first one low.

Video 53: The Best Protection for your Circuit is NOT a Fuse! But a Resettable Fuse?

1. **Limitations of Traditional Fuses:** The document highlights the drawbacks of standard glass fuses, primarily their need for replacement after tripping, which can be "cumbersome," "expensive," and impossible in enclosed electronics like smartphones.
2. **Introduction of Resettable Fuses (PPTCs):** The core theme is the presentation of resettable fuses as a solution to the problems associated with traditional fuses.
3. **Mechanism of Operation:** The document explains that resettable fuses, technically called PPTCs (polymeric positive temperature coefficient devices), work by increasing their resistance as their temperature rises due to overcurrent.
4. **Key Properties of PPTCs:** Crucial parameters for selecting and using PPTCs are identified and explained: Maximum Voltage, Maximum Current, Hold Current, and Trip Current.
5. **Practical Demonstration and Performance:** The document describes experiments illustrating the behavior of PPTCs under different current conditions, including their tripping characteristics and the resulting leakage current.
6. **Comparison with Other Protection Methods:** The document briefly compares PPTCs to traditional fuses and eFuses, emphasizing that each type of protection is suited for specific applications.

Video 54: The Most Important Circuit for our Electrical Future?!

1. **Poor Power Factor in Modern Devices:** The video highlights that many common electronic devices, particularly those with AC to DC power supplies (like LED strips), draw current in a non-sinusoidal manner, often as short pulses near the peak of the mains

voltage. This is in stark contrast to devices like a heat gun, which draws current in phase with the voltage, resulting in a sinusoidal waveform.

- 2. High Apparent Power:** The "weird current waveform" of devices with poor power factor leads to them drawing a significant amount of apparent power from the grid, even if the real power required for their function is relatively small.
- 3. Reactive Power:** This difference between apparent and real power is partly due to reactive power, which "only oscillates between the energy provider and hooked up load." This reactive power is "completely useless" for the user but increases the current flowing through the grid.
- 4. Current Harmonics:** The non-sinusoidal current waveform is also a result of current harmonics – frequencies that are multiples of the fundamental mains frequency (e.g., 150Hz, 250Hz, 350Hz for a 50Hz fundamental). These harmonics also contribute to reactive power and distortion.
- 5. Increased Grid Strain and Cost:** Higher current flow due to poor power factor necessitates thicker wires and more robust infrastructure, leading to increased costs for energy providers. It also reduces the overall efficiency of the grid.
- 6. Future Challenges for the Power Grid:** With "tons of AC to DC power supplies in our homes," the cumulative effect of poor power factor from these devices poses "some big challenges in the future" for the power grid.

Video 55: These 3 Cent Components are actually USEFUL?! (Color Ring Inductor)

1. **Introduction and Identification:** Color ring inductors are a type of inductor, visually resembling resistors, identified by color bands indicating their inductance value. They are presented as a significantly cheaper alternative to other inductor types (power inductors, SMD inductors).
2. **Lack of Comprehensive Datasheets:** A major drawback of color ring inductors, particularly those sold in assortment kits, is the absence of detailed datasheets containing crucial electrical parameters like saturation current. Product descriptions often provide limited information, primarily inductance value and a potentially misleading power rating.
3. **Practical Performance and Limitations:** While visually and functionally like other inductors at a basic level, color ring inductors demonstrate significant limitations in power applications. A practical experiment with a boost converter shows they can only handle a fraction of the current compared to a standard inductor of the same inductance value.
4. **Saturation Current as a Critical Factor:** The source highlights saturation current as a key parameter determining an inductor's ability to handle current without its inductance dropping significantly. Color ring inductors are shown to have a much lower saturation current compared to a standard power inductor.
5. **Suitability for Low Power and Beginner Applications:** Despite their limitations in high-power scenarios, color ring inductors are deemed suitable for low-power applications, oscillators, and signal filters. Their low cost makes them attractive for beginners experimenting with electronics.

Video 56: **Ground is MORE IMPORTANT than you think!**

- 1. Soil as Electrical Conductor:** Plain soil or earth can surprisingly be used as an electrical conductor. Using bigger metal plates to penetrate more soil allows devices like a light bulb to work well with soil as the conductor.
- 2. Importance of Ground:** Ground is considered special and important for electricity and electronics, with many examples like ground wires in AC cables and main distribution boards. These distribution boards are even directly connected to the literal earth through a metal rod.
- 3. Protective Earth Wire:** A normal AC power cable comes with a ground wire, in Germany often the green-yellow PE or Protective Earth wire. The word "protective" indicates its primary function, which is for safety reasons.
- 4. Safety Mechanism:** The earth wire is directly connected to the metal chassis of an appliance like a toaster. If the live wire touches the metal enclosure, touching the chassis can be dangerous as you might be connected to Earth, creating a circuit.
- 5. Protection Devices Activating:** This large current causes protective devices like a circuit breaker and an RCB (Residual Current Breaker) inside the distribution panel to trip. These devices tripping save lives by cutting off power when a fault occurs.
- 6. Physical Earth Connection:** The earth wiring inside a distribution panel leads to a bus bar connected to a thick metal rod pushed deep into the earth. This connection utilizes the earth's ability to conduct electricity, although resistance can vary with conditions like moisture.
- 7. Earth as a Reference:** Earth mass is truly humongous and is defined as having a potential of 0V. When excess electrons flow into or out of it, its 0V potential does not significantly change, providing a common ground reference potential.

- 8. Preventing Static Electricity:** Connecting metal parts to Earth (earthing) helps to get rid of potentially dangerous static electricity build-up. High electrostatic voltages can shock people or damage sensitive electronics.
- 9. Ground in Schematics:** Ground symbols in circuit schematics usually signify connection to a common potential point, often the 0V reference for DC voltage. This concept likely spilled over from the idea of Earth being a large 0V reference potential.

Video 57: This Component solves "All" Motor Problems?! (Motor Encoder)

- 1. Introduction to Encoders:** The fundamental purpose of encoders is to measure movement and position, transforming mechanical motion into electrical signals.
- 2. Limitations of Traditional Encoders:** Mechanical and simple optical encoders, while providing basic positional information, often lack the resolution and adaptability for certain motor applications.
- 3. Advantages of Motor Encoders:** Specifically designed or adapted encoders can significantly enhance motor control by enabling precise position and speed feedback, allowing for functionalities like accurate positioning and synchronized movement.
- 4. Different Types of Motor Encoders:** The source highlights mechanical, optical, magnetic, and capacitive encoders, each with varying operating principles, resolutions, and suitability for different applications.
- 5. Motor Control with Encoders:** Encoders are crucial for implementing advanced motor control techniques, such as PID

control, which allows for precise torque, speed, and position management.

- 6. Applications of Motor Encoders:** Examples include creating high-resolution input devices, enabling precise positioning with various motor types (DC, BLDC), and improving the accuracy of robotic systems.

Video 58: This \$0.70 Component SAVES your Circuit?!

- 1. Introduction to Overvoltage and Protection:** Overvoltage events like lightning or electrostatic discharge are rare but can instantly destroy electronics. Protective components are necessary to avoid this damage, integrated into circuits to handle such events.
- 2. Video Scope and Sponsorship:** The video tests if overvoltage components work using high voltage pulses and discusses why some surge protection is more expensive. It is sponsored by Mouser Electronics, where components used in the video were sourced.
- 3. Testing Overvoltage Pulses:** Creating precise overvoltage pulses was attempted using an ESD generator, estimating 15,000V for a 5mm gap. An insulation tester was too safe as its voltage broke down too quickly.
- 4. The Test Circuit:** A cheap microcontroller blink circuit served as the test subject for destruction experiments. These microcontrollers are readily available, inexpensive, and have no other purpose in the lab.
- 5. Transient Voltage Suppressor (TVS):** TVS components, including diode arrays in IC packages, have a symbol like a diode. They connect from a pin to GND to suppress transient voltages.

- 6. TVS Operation and Performance:** TVS components are non-conductive below their reverse stand-off voltage (e.g., 5V) but become highly conductive when voltage increases (e.g., at 6V), clamping the voltage to a maximum value (e.g., 10-12V). They dissipate excess energy as heat and can handle high power pulses, protecting circuits even from increased voltage shocks.
- 7. Metal Oxide Varistor (MOV):** MOVs are capacitor-like components with variable resistance, behaving similarly to bidirectional TVS diodes by clamping voltage¹. They also dissipate the excess energy of overvoltage as heat
- 8. MOV Usage and Effectiveness:** MOVs are frequently used at the AC input of power supplies, sometimes with a thermal fuse. They proved effective in protecting the 5V test circuit despite potentially higher protection values.

Video 59: Is This the NEW GOLDEN Standard for Communication? (I3C):

- 1. Development of a Low-Cost Haptic Feedback Driver:** The source details the process of creating a more affordable alternative to an expensive development board for a haptic feedback system utilizing the BOS1921 IC.
- 2. Introduction and Exploration of I3C:** A significant portion of the source is dedicated to introducing I3C as the successor to the widely used I2C protocol and highlighting its key advantages and differences.
- 3. Comparison of I2C and I3C:** The source directly compares the features and limitations of both I2C and I3C, providing insights into why I3C is considered a "pretty big deal."

- 4. Practical Application and Testing:** The source documents the practical steps involved in designing, assembling, and testing the developed breakout board, including troubleshooting common issues.

Video 60: **The World's Simplest Audio Amp just got BETTER?! (MOSFET Amp)**

- 1. Reviving and Enhancing Simple Audio Amplifier Designs:** The core motivation is to take a previously developed, simple audio amplifier design (originally for headphones) and make it powerful enough to drive a loudspeaker, addressing the obsolescence of wired headphone jacks in modern devices.
- 2. Comparing Transistor Technologies for Amplification:** The video directly compares the performance of a Bipolar Junction Transistor (BJT), a Darlington transistor (essentially two BJTs), and a MOSFET as the active amplifying component in the simple circuit topology.
- 3. Addressing Practical Design Challenges:** The source details the practical issues encountered when scaling up the power output of the simple amplifier, including current handling limitations, voltage drop considerations, component heating, and the need for proper biasing and component selection (resistors, capacitors, heatsinks).
- 4. Evaluating Amplifier Performance:** The comparison between transistor types focuses on key metrics like loudness (current handling), efficiency, and audio fidelity (clipping, distortion).